

Boolean Functions

Motivations

Properties of Digital System ↘ *Boolean Expressions*

Can keep similar sizes

Computer representations

Circuits: smallest known representations

Normal Forms CNF/BDD/...

Lazy normalizations BED/SAT

Exponential risk

Cook's theorem: NP-complete

Real world systems: polynomial normal form?

Applications

Circuit/System/Software Verification

Circuit/Software Synthesis

Non Boolean applications

$b_3 b_2 b_1 b_0$	$\{i : 1=b_i\}$	$b(z)$	$\sum_{k<4} b_k 2^k$	$\sum_{k<3} b_k 2^k - 8b_3$	$f(x,y) = b_{x+2y}$
0000		0	0	0	0
0001	0	1	1	1	$\neg x \ \& \ \neg y$
0010	1	z	2	2	$x \ \& \ \neg y$
0011	0,1	$1+z$	3	3	$\neg y$
0100	2	z^2	4	4	$\neg x \ \& \ y$
0101	0,2	$1+z^2$	5	5	$\neg x$
0110	1,2	$z+z^2$	6	6	$x \ \wedge \ y$
0111	0,1,2	$1+z+z^2$	7	7	$\neg x \ \ \neg y$
1000	3	z^3	8	-8	$x \ \& \ y$
1001	0,3	$1+z^3$	9	-7	$\neg x \ \wedge \ y$
1010	1,3	$z+z^3$	10	-6	x
1011	0,1,3	$1+z+z^3$	11	-5	$x \ \ \neg y$
1100	2,3	z^2+z^3	12	-4	y
1101	0,2,3	$1+z^2+z^3$	13	-3	$\neg x \ \ y$
1110	1,2,3	$z+z^2+z^3$	14	-2	$x \ \ y$

Net-list

Expression

$$\mathcal{E}_i = 0 \mid 1 \mid x_1 \mid \dots \mid x_i \mid$$

$$? e \mid e' \mid e'' \mid \text{mux}(e, e', e'')$$

$$e, e', e'' \mid \mathcal{E}_i$$

Boolean function

$$e \mid i \mid \dots \mid i \mid \mid = 2^{2^i}$$

$$f \mid i \mid j \mid \dots \mid i \mid j \mid \mid = 2^{j2^i}$$

Circuit net-list


$$f(x_1 \dots x_i) = (x_{o_1} \dots x_{o_j})$$

$$[x_{i+1} = e_1 \dots x_{i+n} = e_n]$$

$$e_k \mid \mathcal{E}_{i+k} \text{ ok } \downarrow \{i \neq 1 \dots i+n\}$$


Full Addder

$$a_N + b_N + c_N = s_N + 2r_N$$

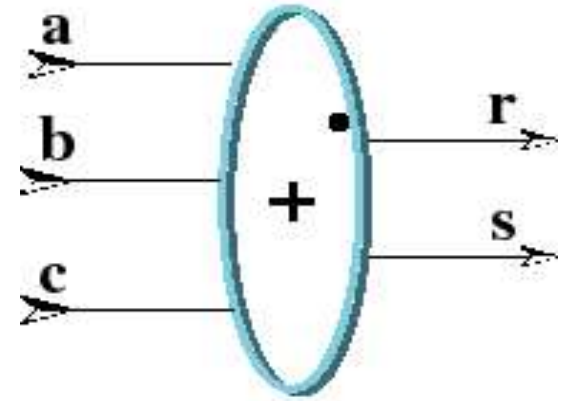

$$s_N = (a_N + b_N + c_N) \mid 2 = a_N \oplus b_N \oplus c_N$$
 
$$r_N = (a_N + b_N + c_N) \gg 2 = a_N b_N \vee b_N c_N \vee c_N a_N$$




$$f[x_1 x_2 x_3] = [x_5 x_6]$$

$$\begin{aligned} ?x_4 &= x_1 \oplus x_2 \quad ? \\ ?x_5 &= x_3 \oplus x_4 \quad ? \\ ?x_6 &= \text{mux}(x_4, x_2, x_3) \end{aligned}$$

$$g[x_1 x_2 x_3] = [x_5 x_8]$$
 
$$\begin{aligned} ?x_4 &= x_2 \oplus x_3 \quad ? \\ ?x_5 &= x_2 \oplus x_3 \quad ? \\ ?x_6 &= x_1 \oplus x_4 \quad ? \\ ?x_7 &= x_1 \oplus x_4 \quad ? \\ ?x_8 &= x_5 \oplus x_7 \quad ? \end{aligned}$$





Example Analysis Task

Logic Circuit Comparison

– **Do circuits compute identical function?**

Basic task of formal hardware verification

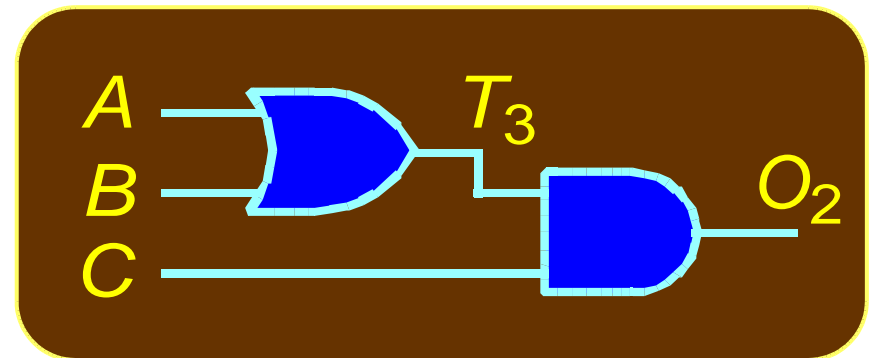 Compare new design to “known good” design




Combinatorial Search

Satisfiability Formulation

- Search for input assignment giving different outputs


Branch & Bound

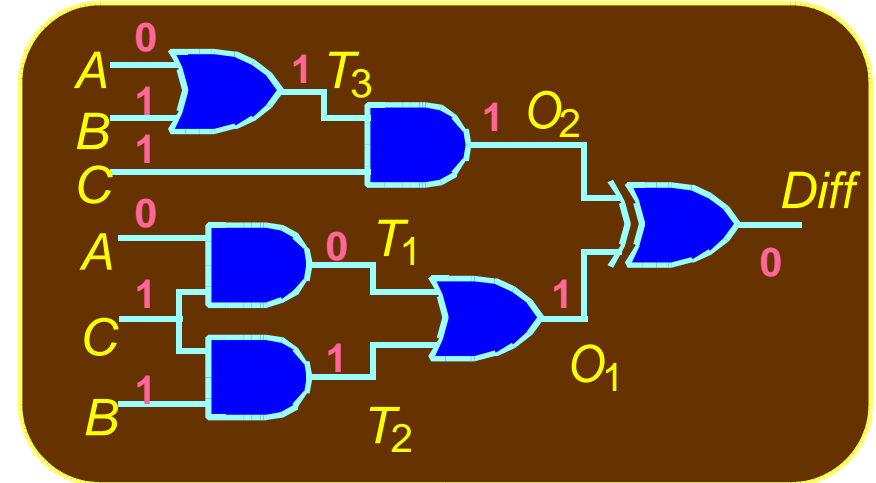- Assign input(s)
- Propagate forced values
- Backtrack when cannot succeed



Challenge




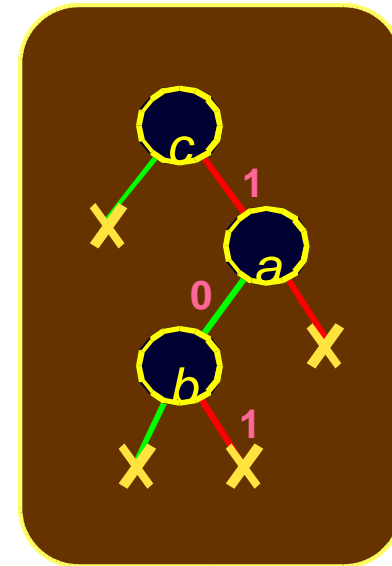
- Must prove all assignments fail
 - ❖ Co-NP complete problem
- Typically explore significant fraction of inputs
- Exponential time complexity



Alternate Approach

Generate Complete Representation of Circuit Function

- Compact, canonical form

    

- Functions equal if and only if representations identical
- Never enumerate explicit function values
- Exploit structure & regularity of circuit functions

Truth Table Language

x_1	0	0	0	0	1	1	1	1
x_2	0	0	1	1	0	0	1	1
x_3	0	1	0	1	0	1	0	1
e	0	0	0	1	0	1	0	1

truth $e = 2^3 + 2^5 + 2^7 = 168$

lang $e = \{011, 101, 111\} = \{3, 5, 7\}$

truth $f = \text{truth } g ?$ **lang** $f = \text{lang } g ?$ $f = g$

truth $f ? [0, 2^{2^i} - 1]$ **truth** $f = \left| f(b_0 \dots b_{i-1})2^n : n = \bigvee_k b_k 2^k \right.$

lang $f ? 2^i$ **lang** $f = \{w ? B^i : f(w_1 \dots w_i) = 1\}$

Normal Forms

x_1	x_2	x_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

DNF (OR-AND)

$$\begin{aligned}f &= x_1'x_2x_3 + x_1x_2'x_3 + x_1x_2x_3 \\ &= x_1'x_2x_3 + x_1x_3\end{aligned}$$

CNF (AND-OR)

$$\begin{aligned}f &= (x_1+x_2+x_3)(x_1+x_2+x_3') \\ &\quad (x_1+x_2'+x_3)(x_1'+x_2+x_3)(x_1'+x_2'+x_3)\end{aligned}$$

ENF (XOR-AND)

$$f = x_1x_3 + x_2x_3 + x_1x_2x_3$$

Cook's Theorem

$$\exists x_1 \dots x_n \quad \bigwedge_{k=1}^n s_k$$

SAT-CNF $s_k = l_{k_1} \mid l_{k_2} \mid \dots \mid l_{k_m}$ is **NP-complete**
 $l_{k_m} \mid \{0, x_k, \neg x_k\}$ **Satisfiability**

SAT-DNF and TAUT-CNF in polynomial time

$$\forall x_1 \dots x_n \quad \bigwedge_{k=1}^n p_k$$

TAUT-DNF $p_k = l_{k_1} \mid l_{k_2} \mid \dots \mid l_{k_m}$ is **coNP-complete**
 $l_{k_m} \mid \{1, x_k, \neg x_k\}$ **Tautology**

Plan

- ***Binary Decision Diagrams BDD***
- ***Integer Dichotomy ID***
- ***Word Level Decision Diagrams *BMD***
- ***Symbolic Diagrams TED***

